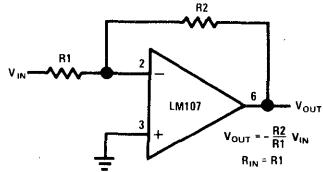





February 1970

op amp circuit collection


section 1 — basic circuits




Inverting Amplifier

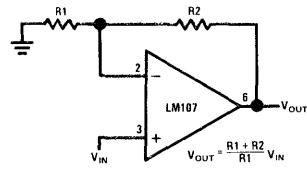


Non-Inverting Amplifier

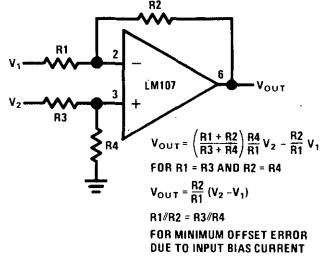


Difference Amplifier

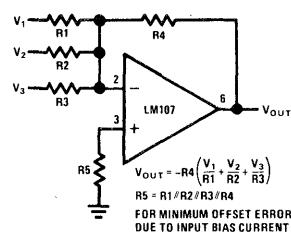


Inverting Summing Amplifier

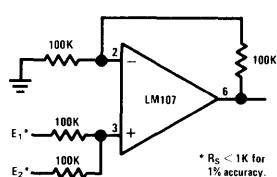


Non-Inverting Summing Amplifier

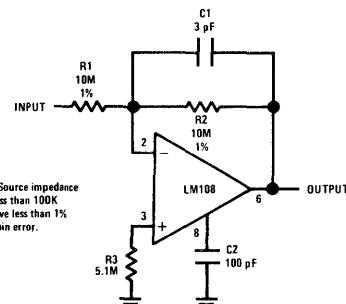

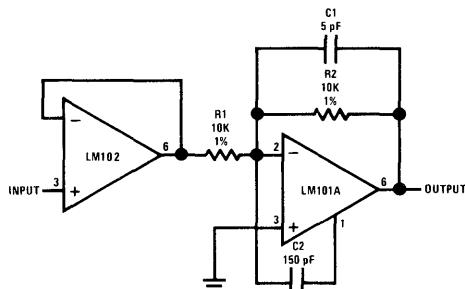
Inverting Amplifier with High Input Impedance



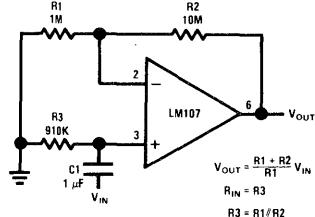
Fast Inverting Amplifier With High Input Impedance




Non-Inverting AC Amplifier

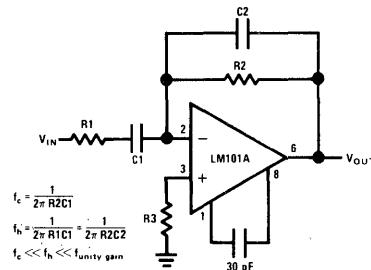


Practical Differentiator

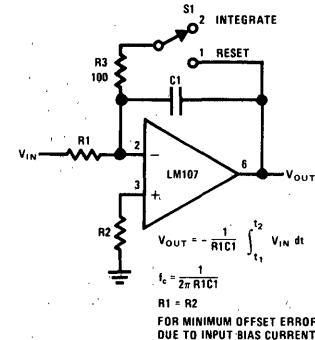


Integrator

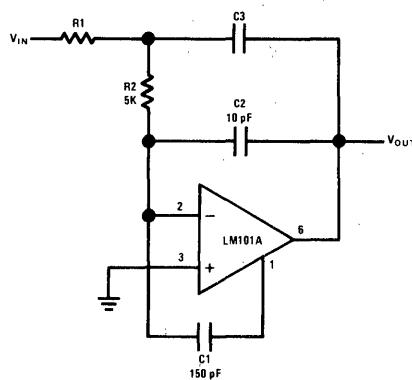


Fast Integrator

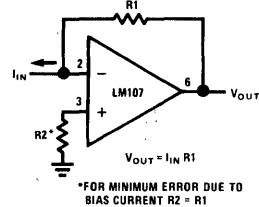


Current to Voltage Converter

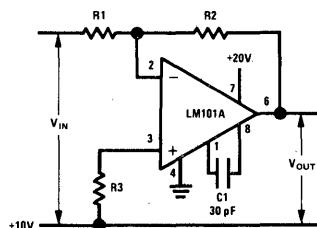

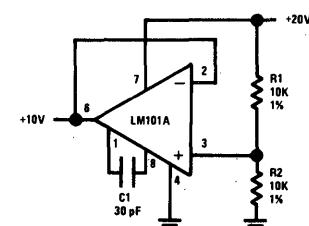
Circuit for Operating the LM101 without a Negative Supply



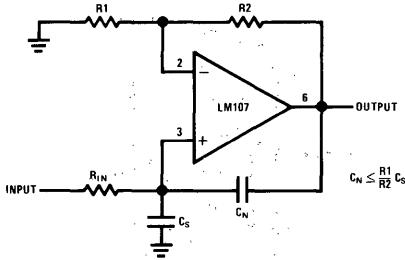
Circuit for Generating the Second Positive Voltage



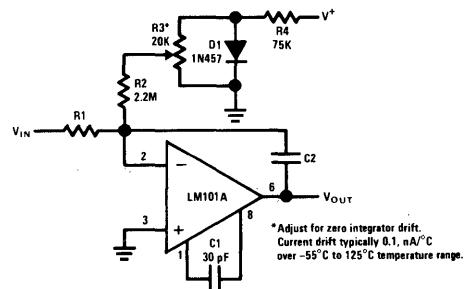
Neutralizing Input Capacitance to Optimize Response Time



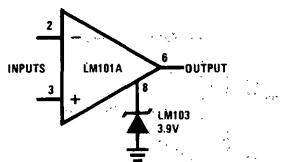
Integrator with Bias Current Compensation



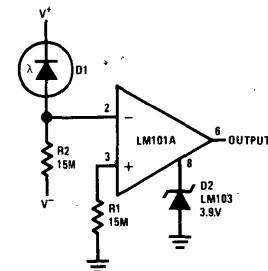
Voltage Comparator for Driving DTL or TTL Integrated Circuits




Threshold Detector for Photodiodes

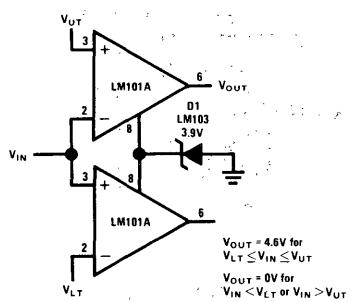

Double-Ended Limit Detector

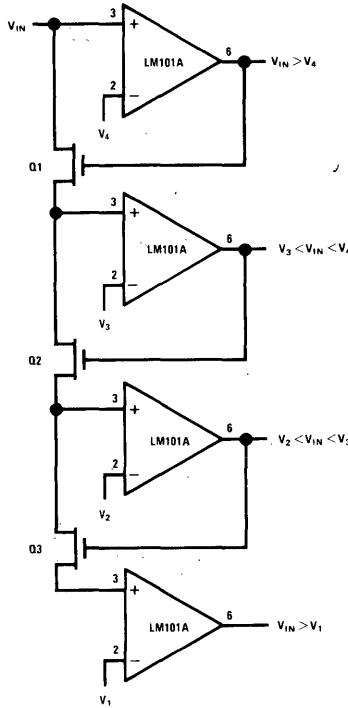


Multiple Aperture Window Discriminator

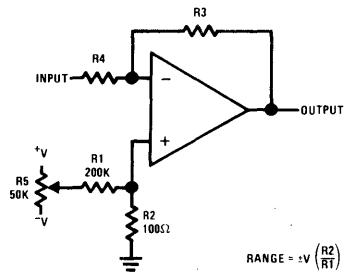


$$\text{RANGE} = \pm V_o \left(\frac{R_2}{R_1} \right)$$

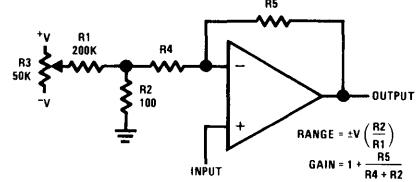Offset Voltage Adjustment for Inverting Amplifiers Using Any Type of Feedback Element




$$\text{RANGE} = \pm V_o \left(\frac{R_2}{R_1} \right)$$

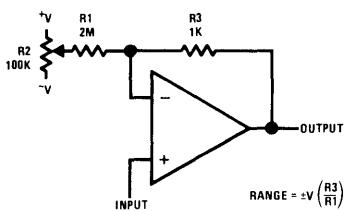Offset Voltage Adjustment for Non-Inverting Amplifiers




$$\text{RANGE} = \pm V_o \left(\frac{R_3}{R_1} \right)$$

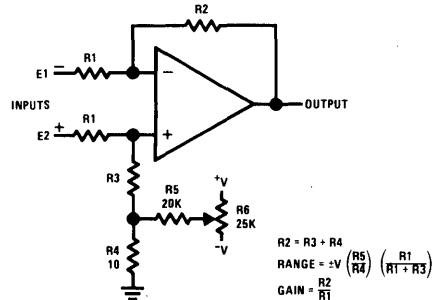Offset Voltage Adjustment for Voltage Followers



$$\text{RANGE} = \pm V_o \left(\frac{R_5}{R_4} \right) \left(\frac{R_1}{R_1 + R_3} \right)$$

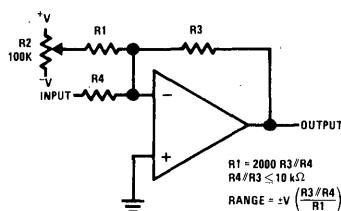
Offset Voltage Adjustment for Differential Amplifiers




$$\begin{aligned} R_1 &= 2000 R_3 / R_4 \\ R_4 / R_3 &\leq 10 \text{ k}\Omega \end{aligned}$$

Offset Voltage Adjustment for Inverting Amplifiers Using 10 kΩ Source Resistance or Less







section 2 — signal generation

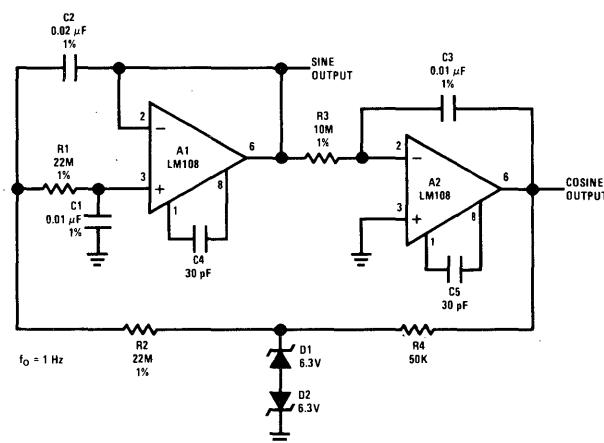


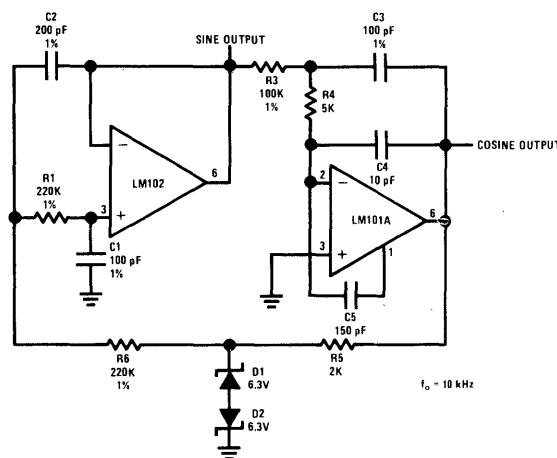Low Frequency Sine Wave Generator with Quadrature Output




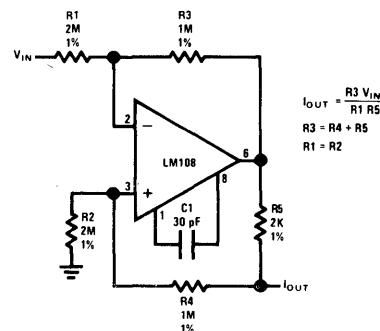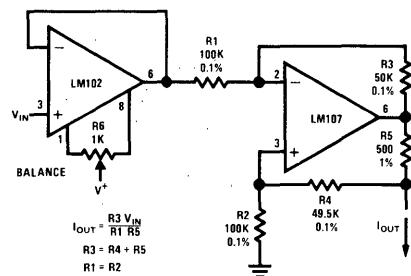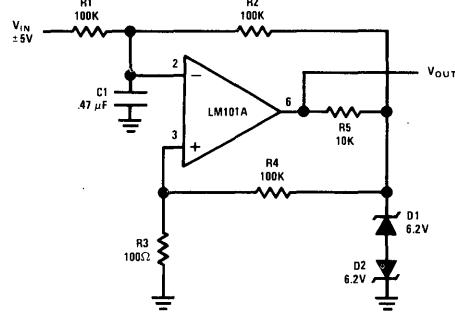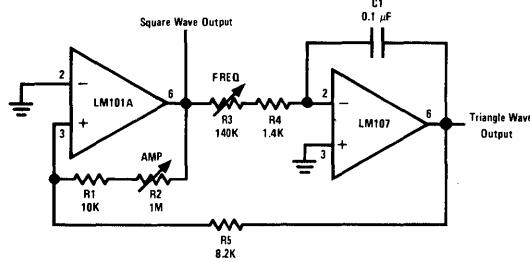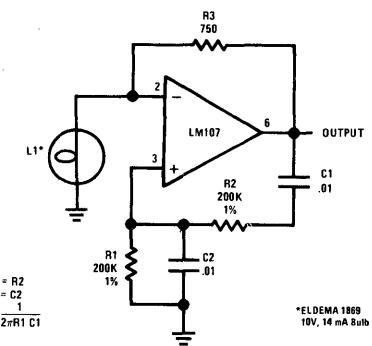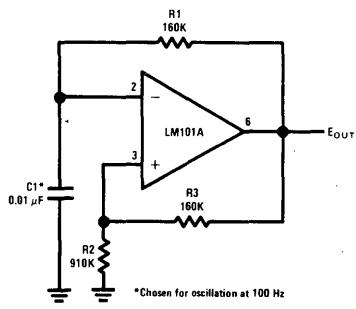High Frequency Sine Wave Generator with Quadrature Output




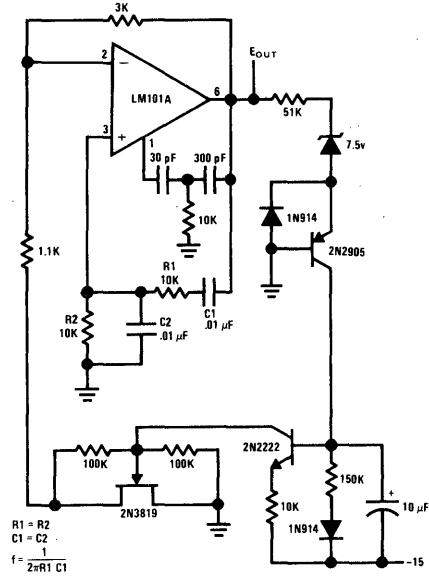

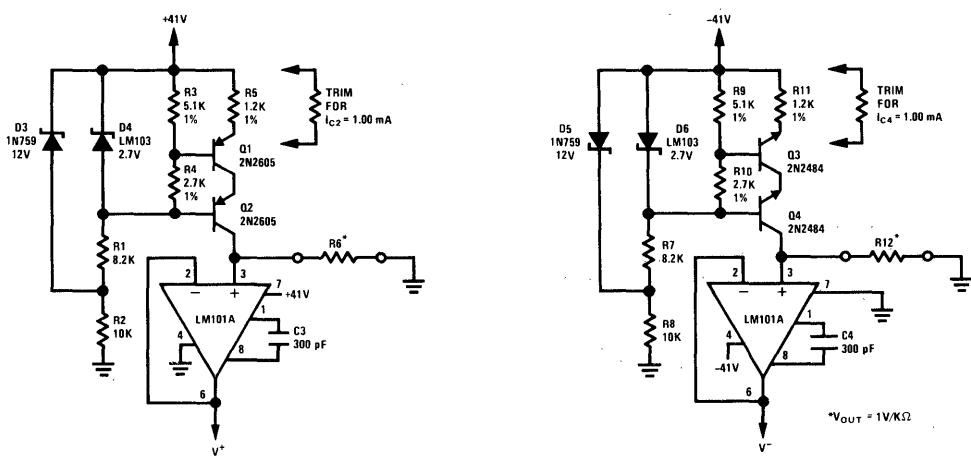
Wein Bridge Oscillator with FET Amplitude Stabilization



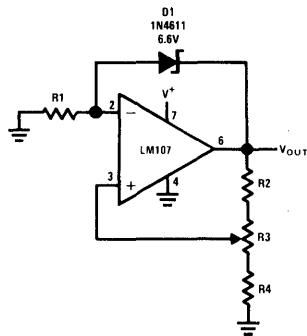
Low Power Supply for Integrated Circuit Testing




Positive Voltage Reference

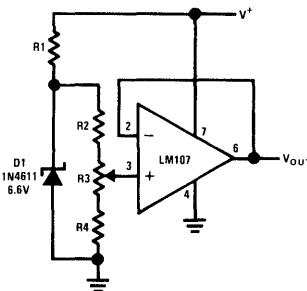


Positive Voltage Reference

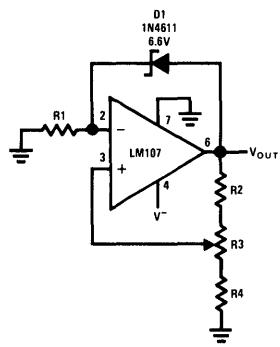


Negative Voltage Reference

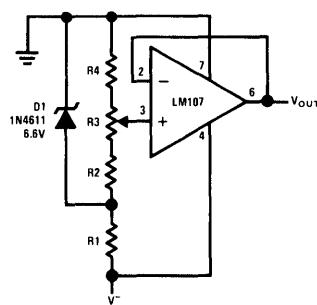

Negative Voltage Reference

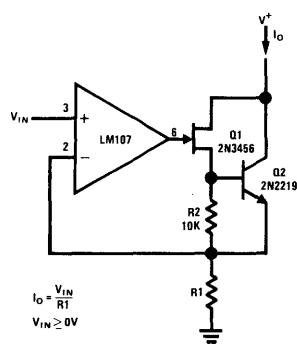


Precision Current Sink

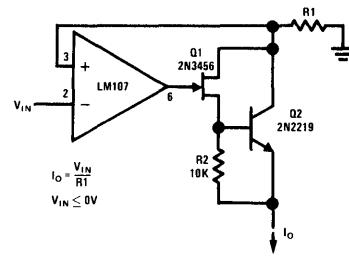


Precision Current Source


section 3 – signal processing

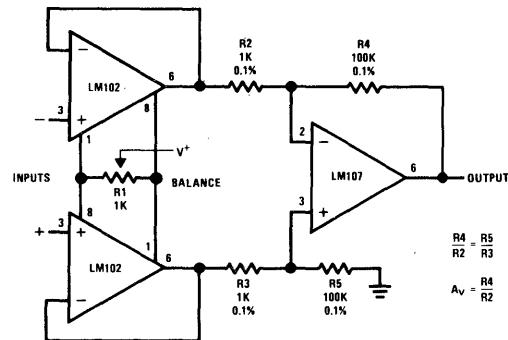

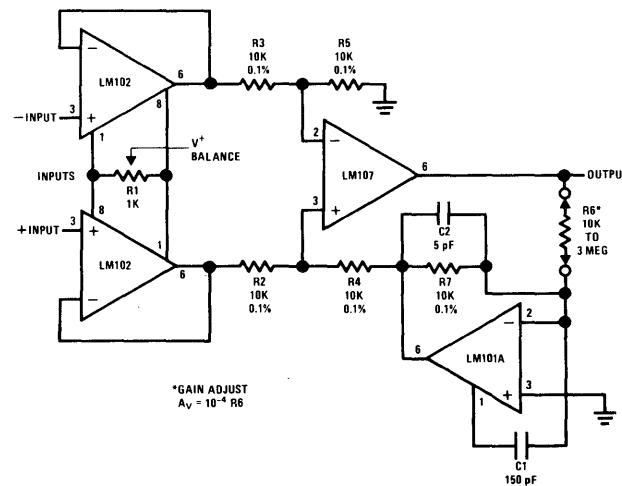
Differential-Input Instrumentation Amplifier



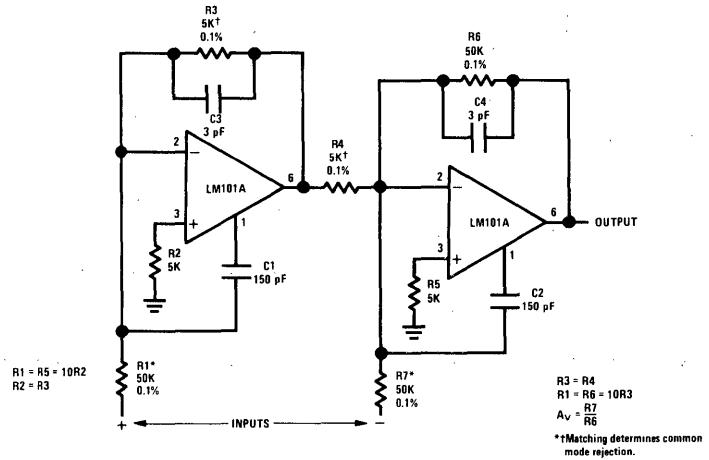
Variable Gain, Differential-Input Instrumentation Amplifier



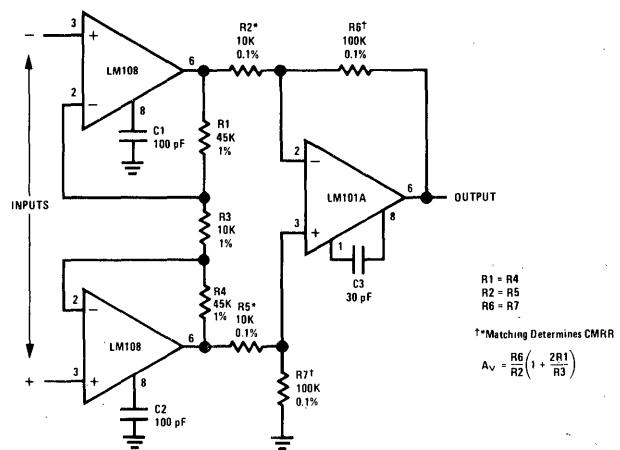
Instrumentation Amplifier with ± 100 Volt Common Mode Range



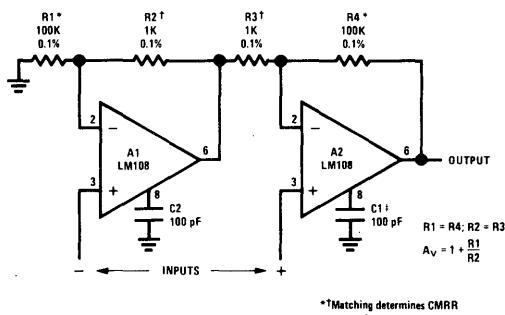
Differential Input Instrumentation Amplifier with High Common Mode Rejection



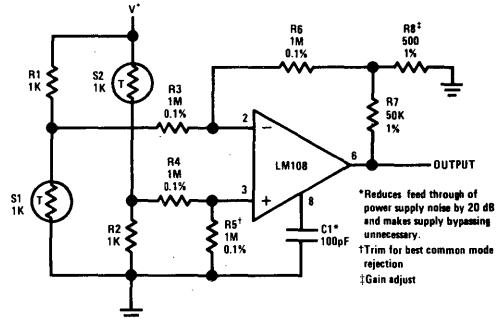
High Input Impedance Instrumentation Amplifier



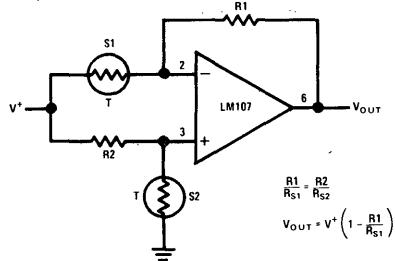
Bridge Amplifier with Low Noise Compensation




Bridge Amplifier

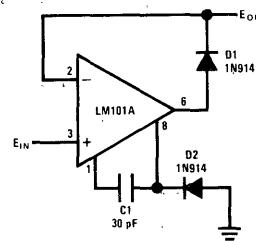


Precision Diode

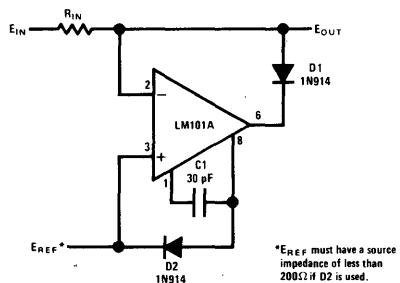


Precision Clamp

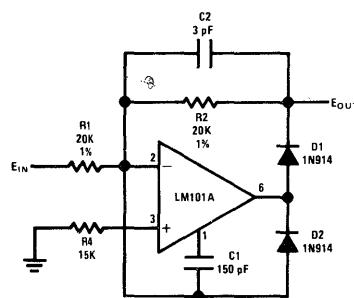


Fast Half Wave Rectifier

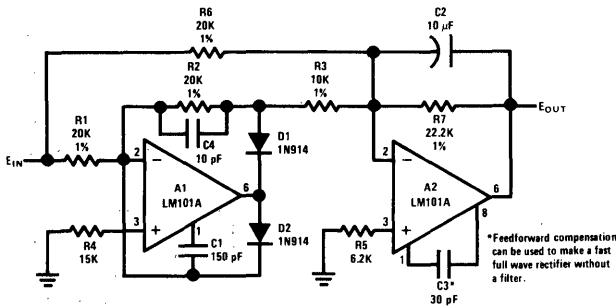


Precision AC to DC Converter

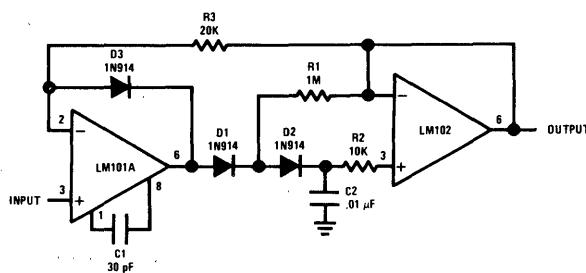


Low Drift Peak Detector

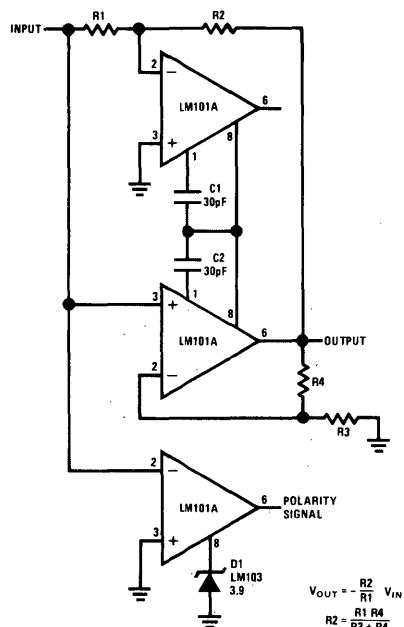

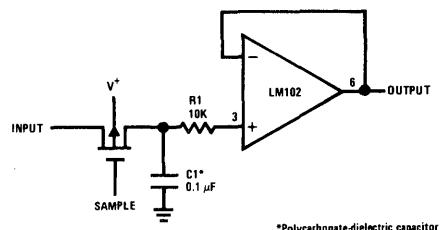
Absolute Value Amplifier with Polarity Detector



Sample and Hold

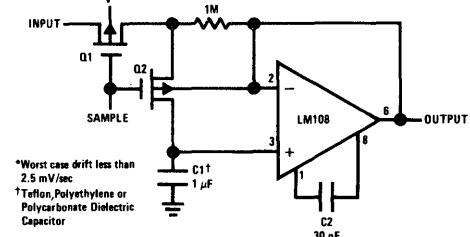


Sample and Hold

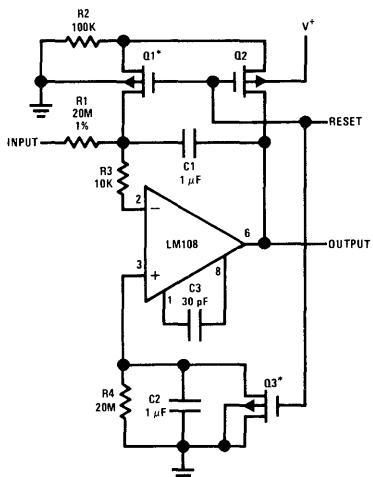

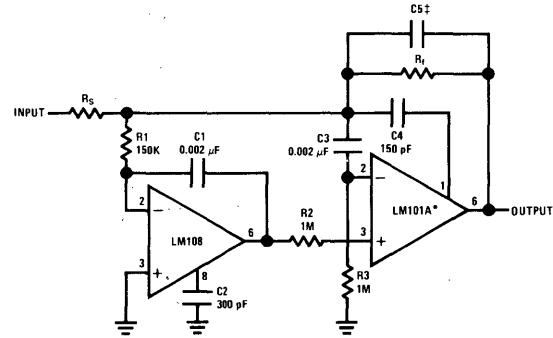*Q1 and Q2 should not have internal gate-protection diodes.

Worst case drift less than
500 μV/sec over -55°C
to +125°C.




† Power Bandwidth: 250 kHz
Small Signal Bandwidth: 3.5 MHz
Slew Rate: 10V/μs


$$\ddagger C_5 = \frac{6 \times 10^{-8}}{R_1}$$

Low Drift Integrator

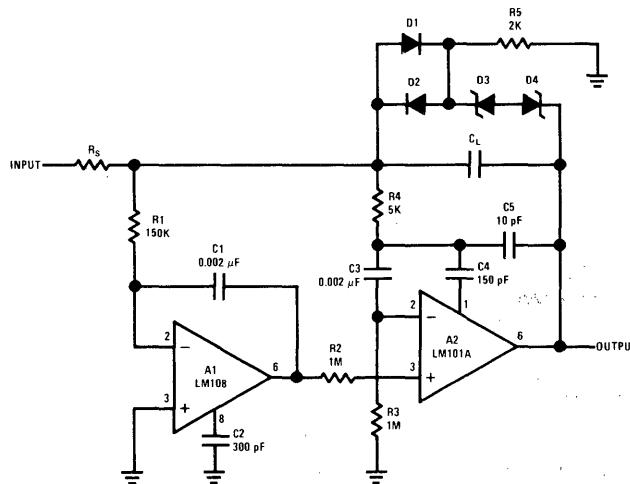
Fast† Summing Amplifier with Low Input Current




Fast Integrator with Low Input Current

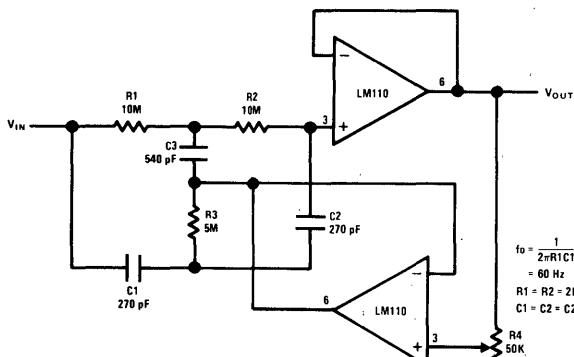


Adjustable Q Notch Filter

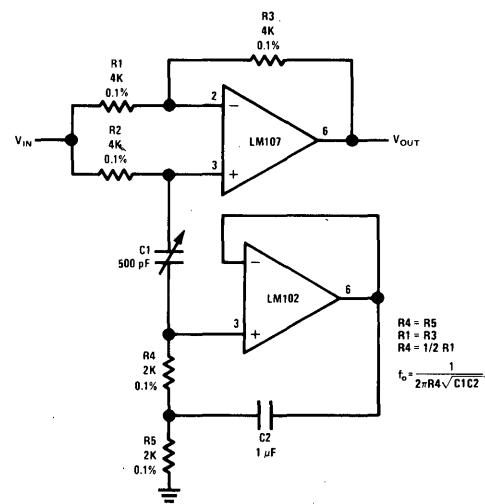


Easily Tuned Notch Filter

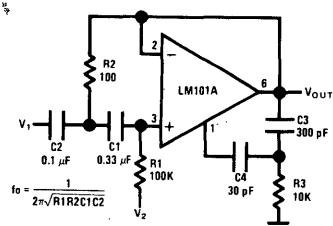


Tuned Circuit

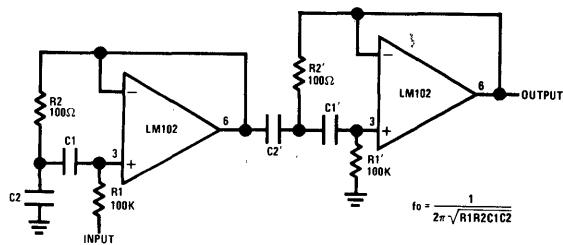


Two-Stage Tuned Circuit

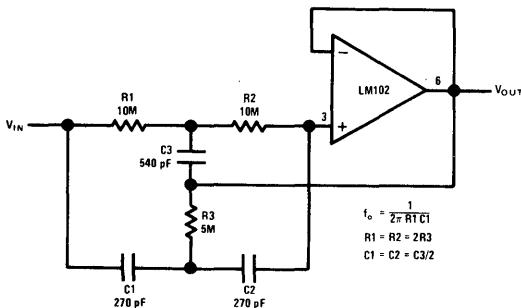


High Q Notch Filter

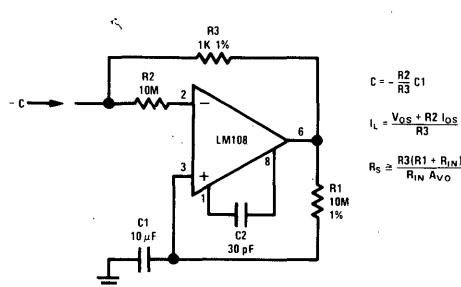


Negative Capacitance Multiplier

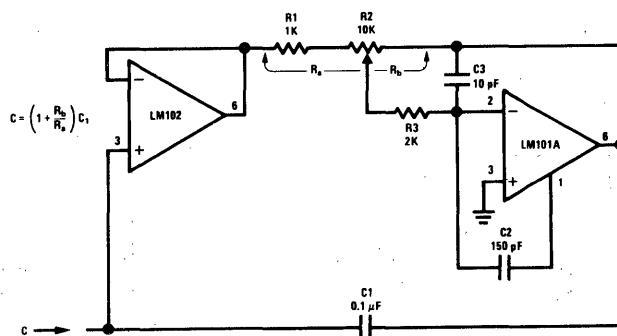


Variable Capacitance Multiplier

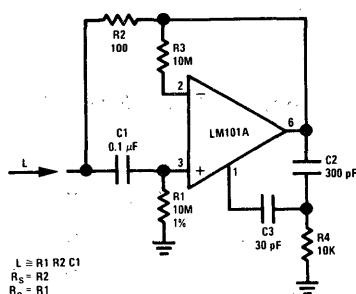


Simulated Inductor

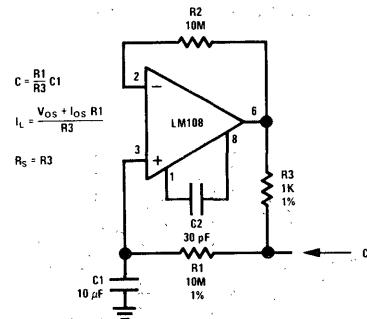


Capacitance Multiplier

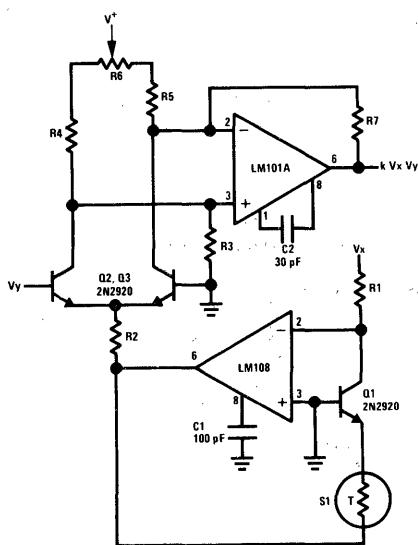


Two Quadrant Multiplier

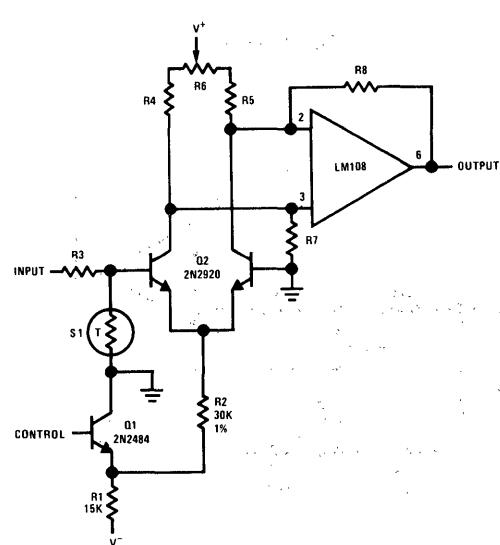


Voltage Controlled Gain Circuit

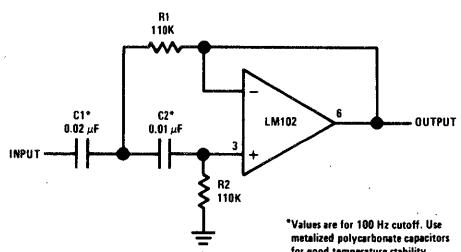


High Pass Active Filter

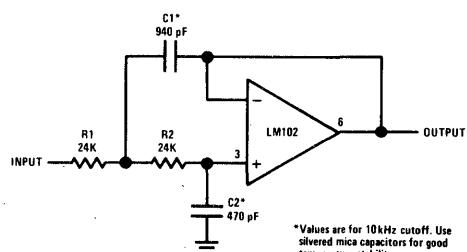


Low Pass Active Filter

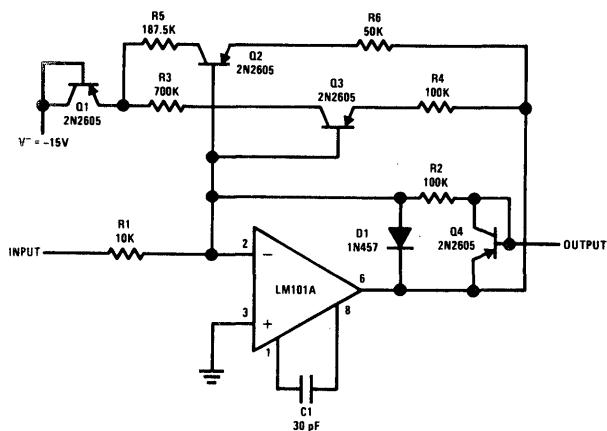

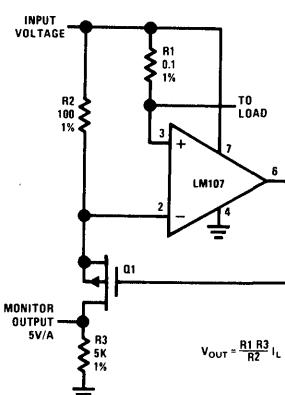
Nonlinear Operational Amplifier with Temperature Compensated Breakpoints




Current Monitor

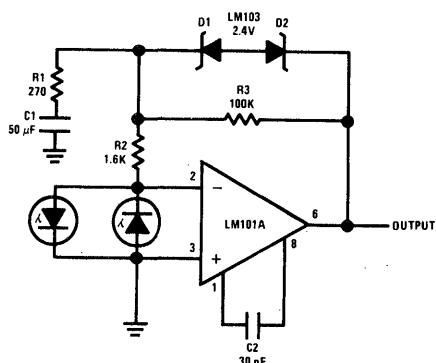

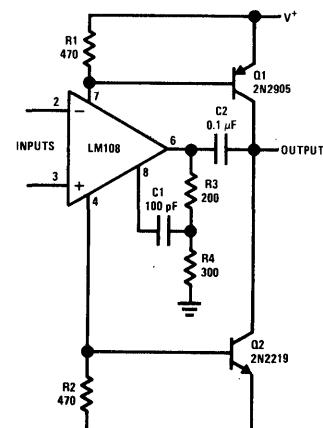
Saturating Servo Preamplifier with Rate Feedback




Power Booster

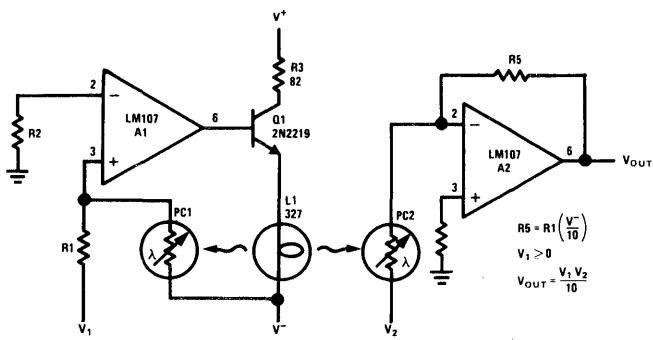


Analog Multiplier

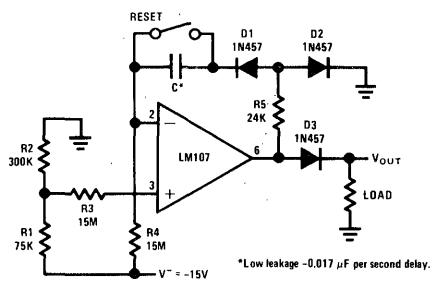


Long Interval Timer

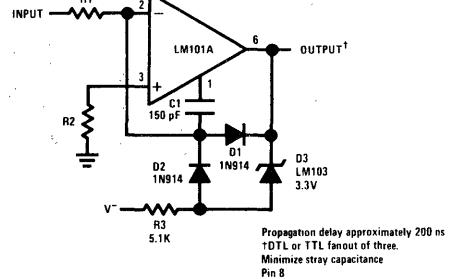


Fast Zero Crossing Detector

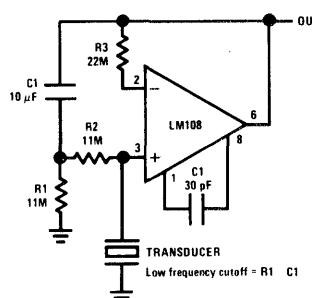

Amplifier for Piezoelectric Transducer

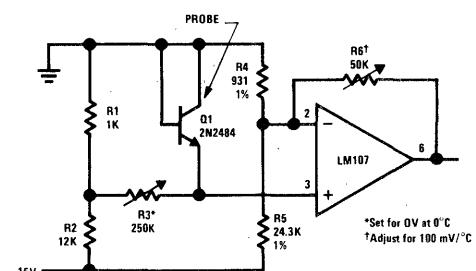


Temperature Probe

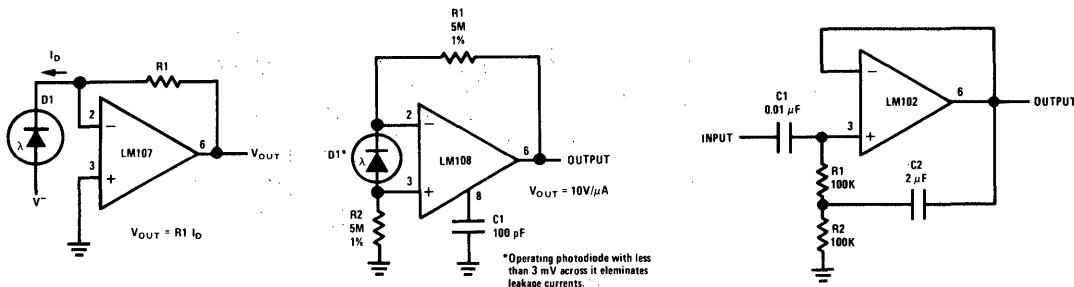

Photodiode Amplifier

Photodiode Amplifier

High Input Impedance AC Follower

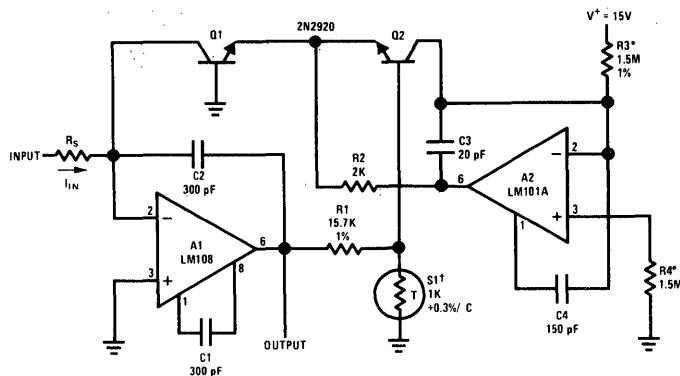


$10 \text{ nA} < I_{IN} < 1 \text{ mA}$
Sensitivity is 1V per decade.

†Available from Tel Labs, Inc., Manchester, N.H., Type 081.


*Determines current for zero crossing on output: $10 \mu\text{A}$ as shown.

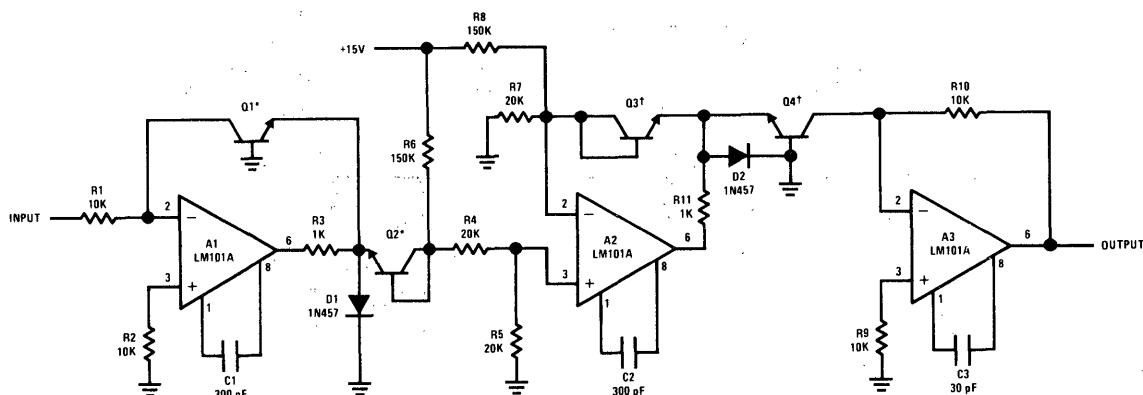Temperature Compensated Logarithmic Converter




* 2N3728 matched pairs


Root Extractor

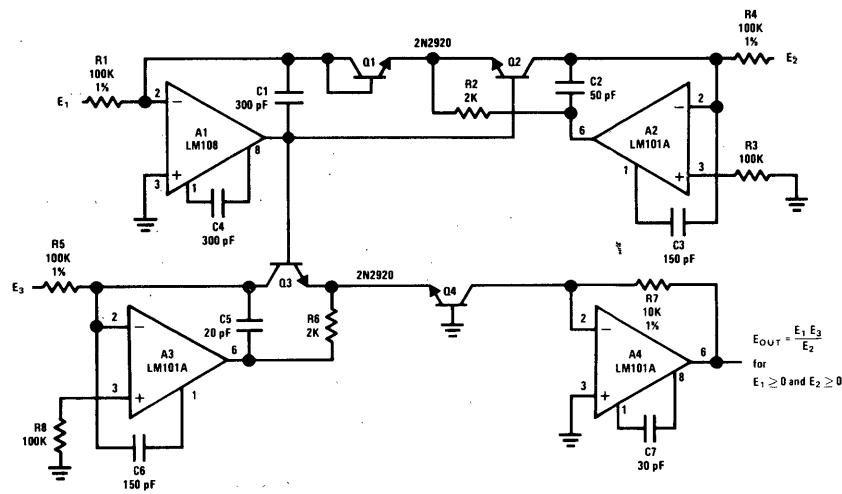

Multiplier/Divider

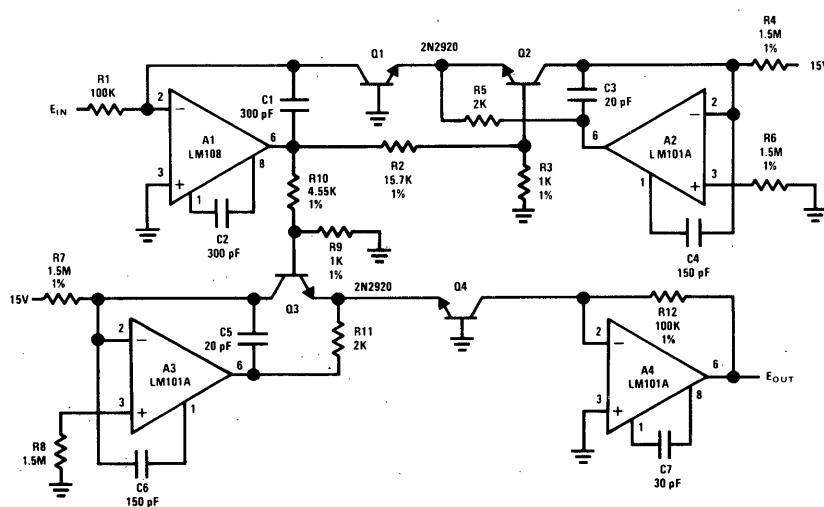


Cube Generator

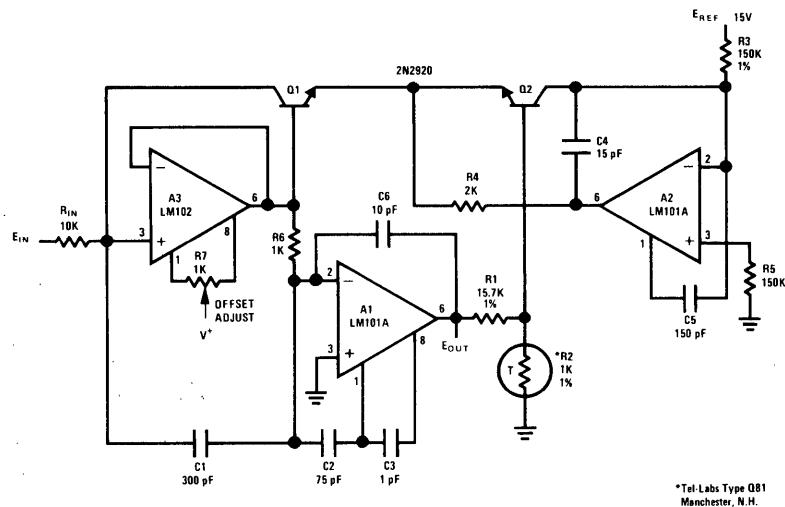

*Tel-Labs Type Q81
Manchester, N.H.

Fast Log Generator

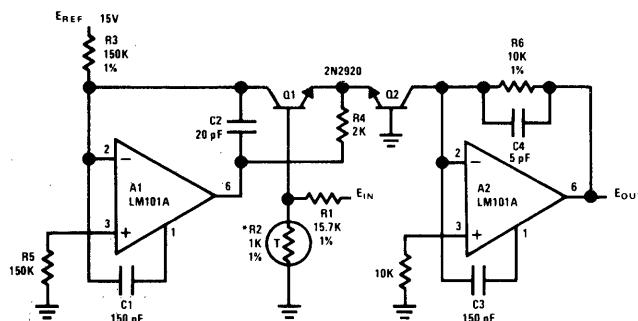

*Tel-Labs Type Q81
Manchester, N.H.

Anti-log Generator